High statistics varistor tests

Donna, Jonathan, Joseph, Hans, Anne

Two measurements:

- 1) Clamping voltage ————— seems straight forward
- 2) Varistor resistance ———— some more thoughts on the next two slides

What we would like to know:

How much does the addition of varistors change the total resistance between the field cage tubes?

Lets say we allow a change of

$$R_{tot}' = x * R_{tot}$$

with x (fractional change) to be specified


$$R_{V} > \frac{\frac{250 \text{ M}\Omega}{\text{N}}}{1/\text{x} - 1}$$


Let's say we allow 1% change \rightarrow x = 0.99

$$R_V > 25 G\Omega / N$$

Let's say we allow 0.1% change -> x = 0.999

$$R_V > 250 G\Omega / N$$

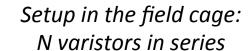

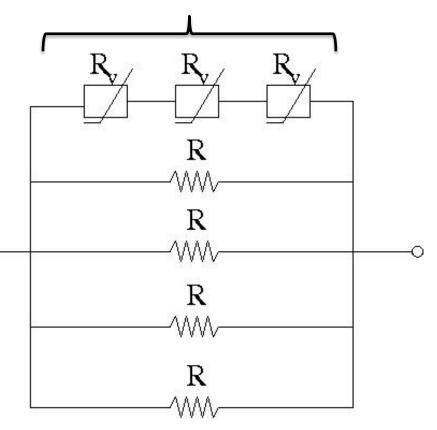


Our test setup:

We measure the voltage V across the $1M\Omega$ resistor:

$$V = \frac{1 \text{ kV} * 1 \text{ M}\Omega}{(R_V + 1 \text{ M}\Omega)}$$

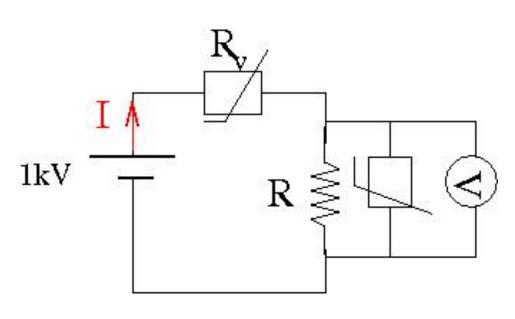This voltage is really small (for $R_V = 10 \text{ T}\Omega \rightarrow V = 0.1 \text{ mV}$)



We will try to measure the resistance. If not possible (fluctuating a lot!) we will classify in categories:

Category 1: V < 1 mV

 $R_V > 1 T\Omega$

x > 0.9998

Category 2: V < 10 mV

 $R_V > 100 G\Omega$

x > 0.998

Category 3: everything else